

EXPERIMENT NO : 01

Half Adder, Full Adder using three modelling styles

Aim :

Develop and verify a Verilog code, exercise a testbench, synthesize, and do the initial timing verification with gate level simulation.

Half Adder :

Theory:

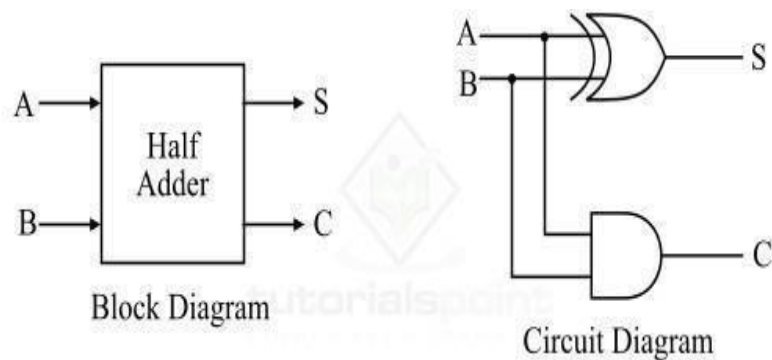


Figure 1 - Half Adder

A half adder is a digital circuit that adds two single binary digits and produces a sum and a carry output. It has two inputs, typically labeled A and B, and two outputs: the sum (S) and the carry (C). The sum is calculated using the XOR operation ($S = A \oplus B$), while the carry is calculated using the AND operation ($C = A \cdot B$).

Truth Table :

Half Adder Truth table

INPUTS		OUTPUTS	
A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder:-

```
module hsfh(a,b, sum,carry);
    input a,b;
    output reg sum,carry;
    always@(a,b)
    begin
        if(a==b)
        begin
            sum=0;
            carry=b;
        end
        else
        begin
            sum=1;
            carry=0;
        end
    end
endmodule
```

Test Bench :-

```
module hfgj_v;

    //Inputs
    reg a;
    reg b;

    // Outputs
    wire sum;
    wire carry;

    // Instantiate the Unit Under Test (UUT)
    hsfh uut (
        .a(a),
        .b(b),
        .sum(sum),
        .carry(carry)
    );

    initial begin
        // Initialize Inputs
        a = 0;
        b = 0;

        // Wait 100 ns for global reset to finish
        #100;
```

```


a = 0;
b = 1;
#100;
a = 1;
b = 0;
#100;
a = 1;
b = 1;
#100;

// Add stimulus here

end
endmodule


```

Output :-

 

Full Adder :

Theory :

 

A full adder is a digital circuit that adds three binary digits: two significant bits and a carry-in bit from a previous addition. It produces a sum and a carry-out, using the equations $S = A \oplus B \oplus C_{in}$ for the sum and $C = (A \cdot B) + (C_{in} \cdot (A \oplus B))$ for the carry-out. This allows it to handle multi-bit binary addition effectively.

Truth Table :

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full Adder :-

```
module fgvc(a,b,cin,sum,carry);
  input a,b,cin;
  output reg sum,carry;
  always@(a,b,cin)
  begin
    if(a==b)
    begin
      sum=cin;
      carry=b;
    end
    else
    begin
      sum=~cin;
      carry=cin;
    end
  end
endmodule
```

Test Bench :-

```
module gff_v;

  //Inputs
  reg a;
  reg b;
  reg cin;

  // Outputs
  wire sum;
  wire carry;
  // Instantiate the Unit Under Test (UUT)
  fgvc uut (
    .a(a),
    .b(b),
    .cin(cin),
    .sum(sum),
    .carry(carry)
  );

  initial begin
    // Initialize Inputs
    a = 0;
    b = 0;
    cin = 0;
```

```

// Wait 100 ns for global reset to finish
#100;
a = 0;
b = 0;
cin =1;
#100;
a = 0;
b = 1;
cin =0;
#100;
// Add stimulus here

```

```

end
endmodule

```

Output :-



EXPERIMENT NO : 02


Flip Flops

AIM :

Develop and verify a Verilog code, exercise a testbench, synthesize, and do the initial timing verification with gate level simulation.

SR Flip Flops :

Theory :

 

An SR flip-flop is a bistable multivibrator that has two inputs, Set (S) and Reset (R), and two outputs, Q and Q' . When S is activated, Q is set to high, while activating R sets Q to low; if both inputs are low, the output retains its previous state. This flip-flop is used for storing binary information and is fundamental in memory storage and sequential logic circuits.

Truth Table :

S	R	Q_{n+1}
0	0	Q_n (No Change)
0	1	0
1	0	1
1	1	x

SR Flip-Flop :-

```
module rfdc(clk,s,r, q,qb);
  input clk,s,r;
  output reg q,qb;
  always@(posedge clk)
  begin
    if(s==0 && r==1)
      q=1'b0;
    else if(s==1 && r==0)
      q=1'b1;
    qb=~q;
  end
endmodule
```

Test Bench :-

```
module thfg_v;

  // Inputs
  reg clk;
  reg s;
  reg r;

  // Outputs
  wire q;
  wire qb;

  // Instantiate the Unit Under Test (UUT)
  rfdc uut (
    .clk(clk),
    .s(s),
    .r(r),
    .q(q),
    .qb(qb)
  );
  always#10 clk=~clk;

  initial begin
    // Initialize Inputs
    clk=0;
    s=0;
    r=0;
    // Wait 100 ns for global reset to finish
    #100;
```




```
clk=1;
s=1;
r=0;
#100;
clk=0;
s=0;

r=1;
#100;
// Add stimulus here
```


```
end
endmodule
```

Output :-

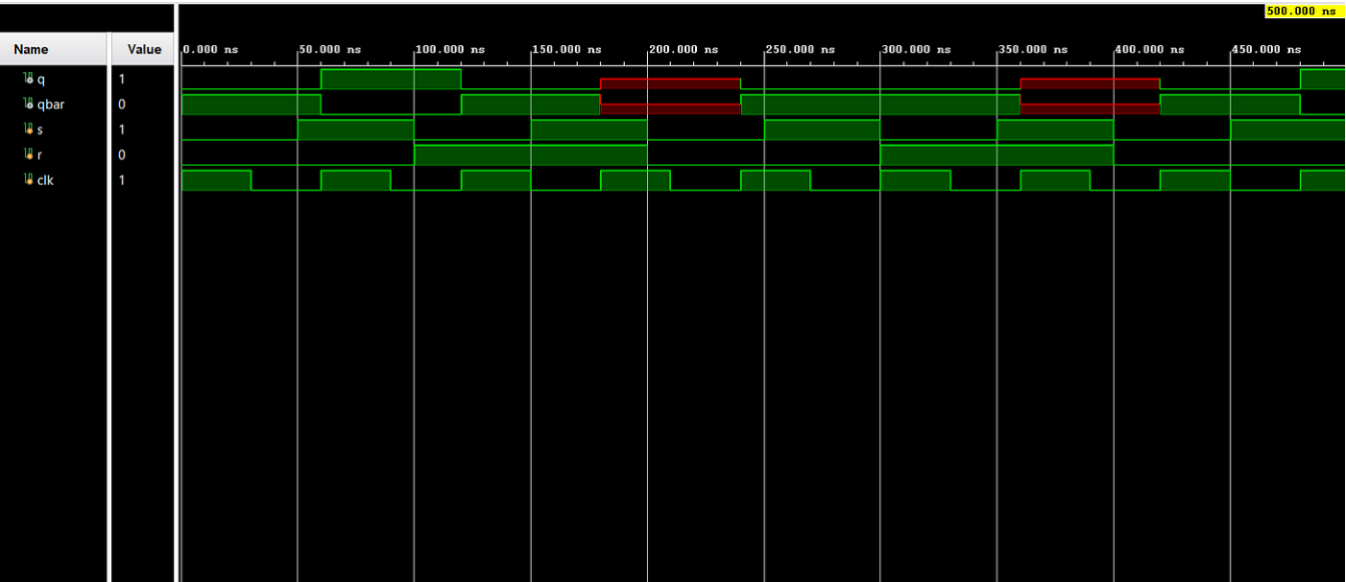

JK Flip Flops:

Theory :

 

A JK flip-flop is a type of bistable multivibrator with two inputs, J and K, and two outputs, Q and Q' . It toggles its output state when both J and K are high, while setting Q high occurs when J is high and K is low, and resetting Q occurs when J is low and K is high. This versatility allows JK flip-flops to be used in counters and various sequential logic applications.

Truth Table :

Clk	J	K	Q	Q'	State
1	0	0	Q	Q'	No change in state
1	0	1	0	1	Resets Q to 0
1	1	0	1	0	Sets Q to 1
1	1	1	-	-	Toggles

JK Flip-Flop :-

```
module frdvc(clk,j,k, q,qb);
  input clk,j,k;
  output reg q,qb;
  always@(posedge clk)
  begin
    if(j==0&&k==0)
      q=0;
    else if(j==0&&k==0)
      q=1'b0;
    else if(j==1&&k==1)
      q=1'b1;
    else
      q=~q;
      qb=~q;
    end
endmodule
```

Test Bench :-


```
module trgf_v;
  // Inputs
  reg clk;
  reg j;
  reg k;
  // Outputs
  wire q;
  wire qb;
  // Instantiate the Unit Under Test (UUT)
  frdvc uut (
    .clk(clk),
    .j(j),
    .k(k),
    .q(q),
    .qb(qb)
  );
  always#10 clk=~clk;
  initial begin
    // Initialize Inputs
    clk = 0;
    j = 0;
    k = 0;

    // Wait 100 ns for global reset to finish
    #100;
```

```
        clk = 1;
        j = 0;
        k = 1;
        #100;
        clk = 1;
        j = 1;
        k = 1;
        #100;
        // Add stimulus here


    end
endmodule
```

Output :-

 

D Flip Flops :

Theory :

 

A D flip-flop is a bistable device that captures the value of the input data (D) on the rising (or falling) edge of a clock signal, transferring it to the output Q. When the clock edge occurs, Q takes on the value of D, while Q^{-} becomes its complement. This simplicity makes D flip-flops essential for data storage, timing applications, and building registers in digital circuits.

Truth Table :

Clock	D	Q	Q'	Description
↓ » 0	X	Q	Q'	Memory no change
↑ » 1	0	0	1	Reset Q » 0
↑ » 1	1	1	0	Set Q » 1

D Flip-Flop :-

```
module gtfbv(clk,rst_n,d, q);
  input clk,rst_n,d;
  output reg q;
  always@(posedge clk or negedge rst_n)
  begin
    if(!rst_n)q<=0;
    else
      q<=d;
    end
endmodule
```

Test Bench :-

```
module yhg_v;

  // Inputs
  reg clk;
  reg rst_n;
  reg d;

  // Outputs
  wire q;

  // Instantiate the Unit Under Test (UUT)
  gtfbv uut (
    .clk(clk),
    .rst_n(rst_n),
    .d(d),
    .q(q)
  );
  always#10 clk=~clk;


  initial begin
    // Initialize Inputs
    clk = 0;
    rst_n = 0;
    d = 0;

    // Wait 100 ns for global reset to finish
    #100;
    clk =1;
    rst_n =1;
    d = 1;
  end
endmodule
```

```
// Add stimulus here
```


```
end  
endmodule
```

Output :-

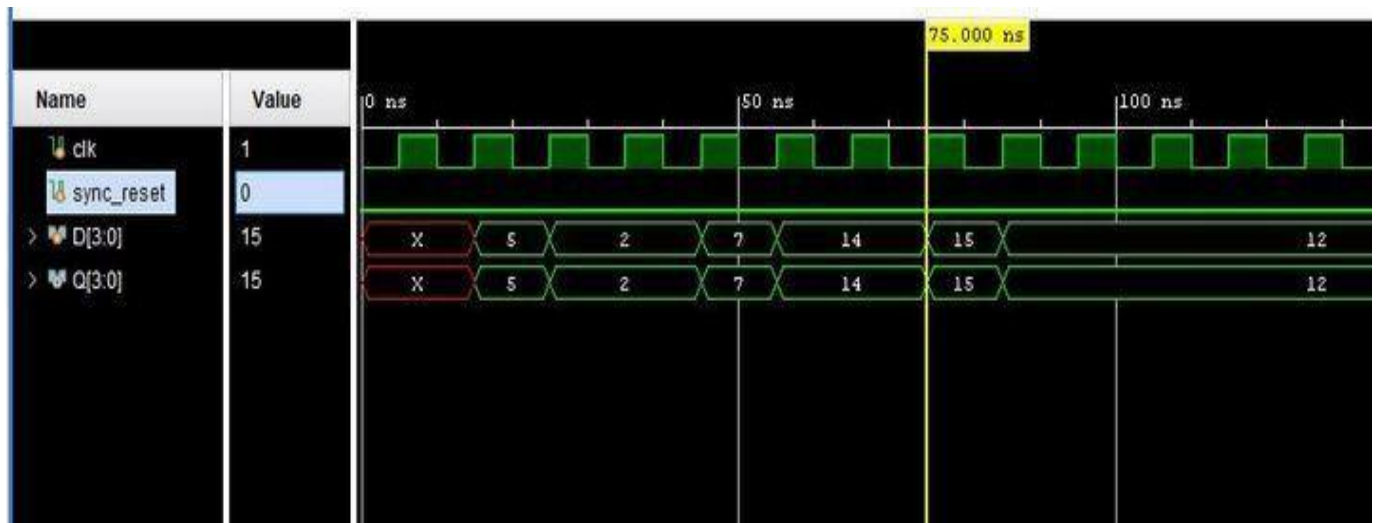

T Flip Flops :

Theory :

 

A T flip-flop, or toggle flip-flop, is a bistable device that changes its output state (toggles) when the T input is high at the clock edge. If T is low, the output remains unchanged. This characteristic makes T flip-flops useful for counting applications and building frequency dividers in digital circuits.

Truth Table :

CLK	T	Q_n	Q_{n+1}
↓	0	0	0
↓	0	1	1
↓	1	0	1
↓	1	1	0

T Flip-Flop :-

```
module refdvc(clk,rst,t, q);
  input clk,rst,t;
  output reg q;
  always@(posedge clk)
  begin
    if(!rst)
      q<=0;
    else
      if(t)
        q<=~q;
      else
        q<=q;
  end
endmodule
```

Test Bench :-

```
module fgh_v;

  // Inputs
  reg clk;
  reg rst;
  reg t;

  // Outputs
  wire q;

  // Instantiate the Unit Under Test (UUT)
  refdvc uut (
    .clk(clk),
    .rst(rst),
    .t(t),
    .q(q)
  );
  always#10 clk=~clk;

  initial begin
    // Initialize Inputs
    clk = 0;
    rst = 0;
    t = 0;


    // Wait 100 ns for global reset to finish
    #100;
```

```
clk =1;  
rst =1;  
t=1;  
#100;
```

```
// Add stimulus here
```

```
end  
endmodule
```

Output :-

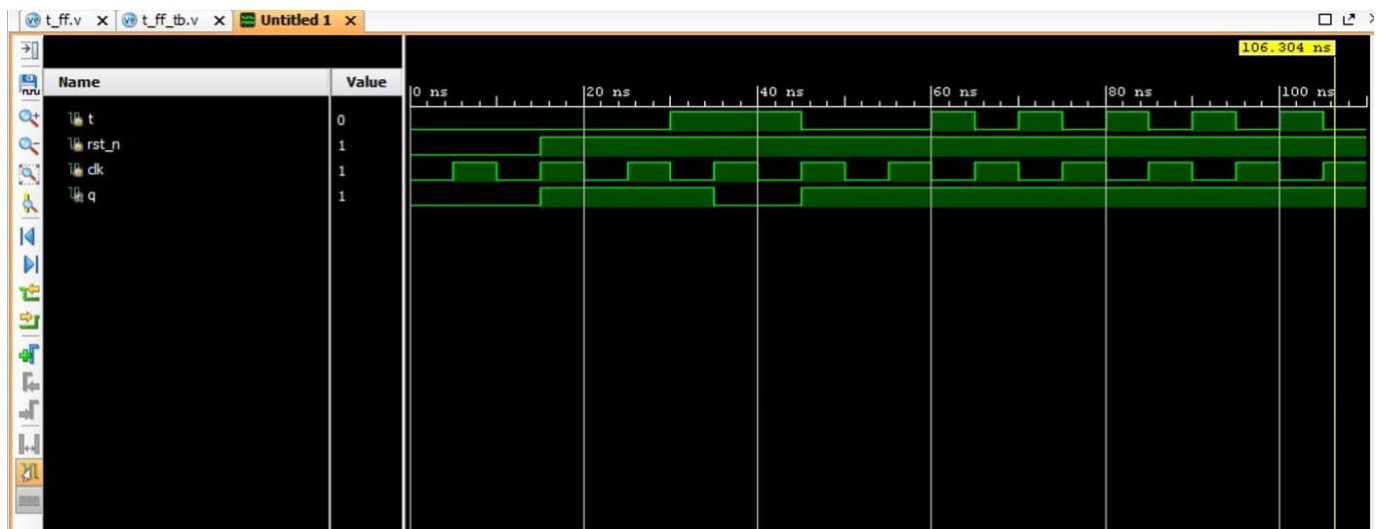


EXPERIMENT NO : 03

N-Bit Comparator

Aim :

Develop and verify a Verilog code, exercise a testbench, synthesize, and do the initial timing verification with gate level simulation.

Theory :

 

An n-bit comparator is a digital circuit that compares two n-bit binary numbers and determines their relative equality or order. It produces outputs indicating whether the first number is less than, equal to, or greater than the second number. Comparators are essential in decision-making circuits, arithmetic operations, and digital systems for sorting and control functions.

Truth Table :

A	B	A<B	A=B	A>B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

N-Bit Comparator :-

```
module fgd(a,b, eq,lt,gt);
  input [3:0] a,b;
  output reg eq,lt,gt;
  always@(a,b)
  begin
    if(a==b)
    begin
      eq=1'b1;
      lt=1'b0;
      gt=1'b0;
    end
    else if(a>b)
    begin
      eq=1'b0;
      lt=1'b0;
      gt=1'b1;
    end
    else
    begin
      eq=1'b0;
      lt=1'b1;
      gt=1'b0;
    end
  end
endmodule
```

Test Bench :-

```
module gfvc_v;

  // Inputs
  reg [3:0] a;
  reg [3:0] b;

  // Outputs
  wire eq;
  wire lt;
  wire gt;

  // Instantiate the Unit Under Test (UUT)
  fgd uut (
    .a(a),
    .b(b),
    .eq(eq),
    .lt(lt),
    .gt(gt)
  );
endmodule
```

```

        .gt(gt)
    );

    initial begin
        // Initialize Inputs

        a =1000;
        b =1000;

        // Wait 100 ns for global reset to finish
        #100;
        a =1000;
        b =0001;

        // Wait 100 ns for global reset to finish
        #100;
        a =0001;
        b =1000;


        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here


    end
endmodule

```

Output :-

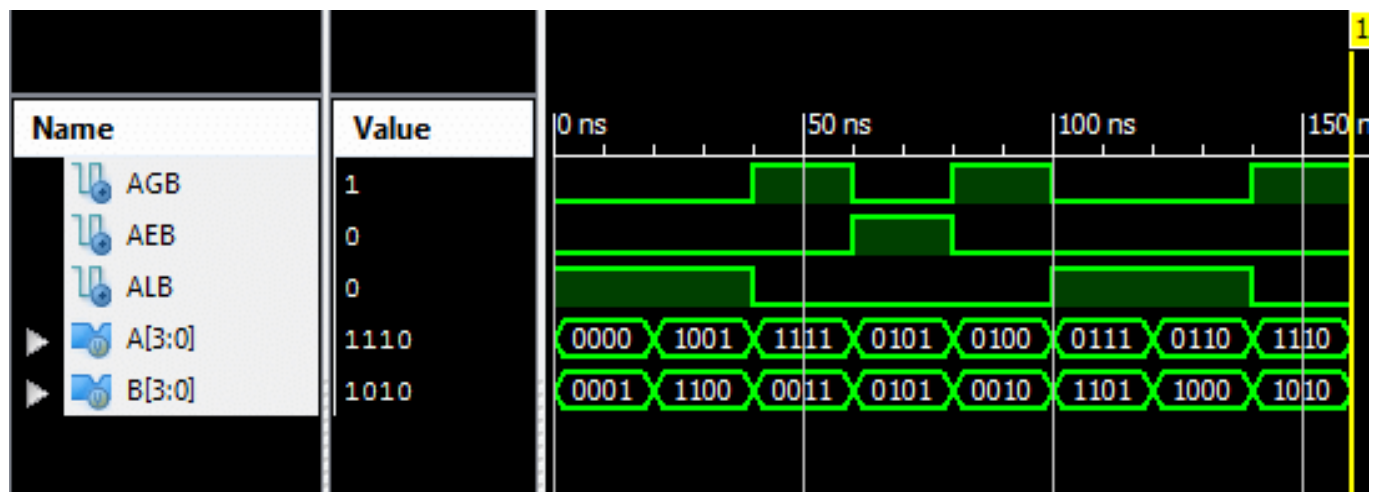

EXPERIMENT NO : 04


DECODER AND ENCODER

Aim:

Develop and verify a Verilog code, exercise a testbench, synthesize, and do the initial timing verification with gate level simulation.

a) 3:8 Decoder:

Theory :

 

A 3:8 decoder is a digital circuit that converts a 3-bit binary input into one of eight unique outputs, with only one output being activated (high) for each combination of input values. It achieves this by using the input bits to select the corresponding output line based on the binary representation of the input. This type of decoder is commonly used in memory addressing, data demultiplexing, and signal routing in digital systems.

Truth Table :

Enable	INPUTS			Outputs							
E	A ₂	A ₁	A ₀	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Decoder :-

```
Module decoder 3_8(in,out,en);
input[2:0] in;
input reg en;
output[7:0] out;
always@ (in or en)
begin
if (en) begin
out = 8'd0;
case(in)
3'b000:out[0]=1'b1;

3'b001:out[1]=1'b1;

3'b010:out[2]=1'b1;

3'b011:out[3]=1'b1;

3'b100:out[4]=1'b1;

3'b101:out[5]=1'b1;

3'b110:out[6]=1'b1;

3'b111:out[7]=1'b1;

default:out=8'd0;
endcase
end
else
out=8'd0;
end
endmodule
```

Test Bench:-

```
module ghnhjn_v;

eg [2:0]in;

reg en;

wire [7:0] out;


initial begin

in=000;

en=0;
```

#100;
in=000;
en=1;
#100;
in=001;
en=1;
#100;
in=010;
en=1;
#100;
in=011;
en=1;
#100;
in=100;
en=1;
#100;
in=101;
en=1;
#100;
in=110;
en=1;
#100;
in=111;
en=1;
#100

Output :-

 

Digital Inputs								Binary Output		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

Priority Encoder:-


```
module Priority_encoder (input [7:0] in; Output reg [2:0]
out;
always @(in)
begin
caseX(in)
8'b1xxxxxxx : out=3'b111;
8'b01xxxxxx : out = 3'b110;
8' b001xxxxx: out = 3'b101;
8' b0001xxxx : out =3'b100;
8' b00001xxx : out =3'b011;
8'b000001xx: out =3;b0120;
8'b000000x: out =3'b001;
8'b0000001: out =3'b000;
default = out = 0;

endcase
end
endmodule
```

EXPERIMENT NO : 05

a) 4:1 multiplexer :-

Theory :

 

A 4:1 multiplexer (MUX) is a digital device that selects one of four input signals based on two control or selection lines. It has four data inputs (D_0 , D_1 , D_2 , D_3) and two selection lines (S_1 , S_0). The output, denoted as Y , corresponds to one of the inputs depending on the values of the selection lines. For instance, if $S_1S_0 = 00$, the output is D_0 , if $S_1S_0 = 01$, the output is D_1 , and so on. The selection lines determine which input is passed to the output through logic gates. A 4:1 MUX can be implemented using AND, OR, and NOT gates. It is commonly used in applications like data routing, multiplexing in communication systems, and as a selector in digital circuits.

Truth Table :

INPUTS		Output
S_1	S_0	Y
0	0	A_0
0	1	A_1
1	0	A_2
1	1	A_3

4:1 multiplexer:-

```
module mux(i0,i1,i2,i3,sel,y)
input i0,i1,i2,i3;
input[1:0] sel;
output reg y;
always@(i0 or i1 or i2 or i3 or sel)
begin
case (sel)
2'b00:y=i0;
2'b01:y=i1;
2'b10:y=i2;
2'b11:y=i3;
default:y=0;
endcase
end
endmodule
```

TestBench:-

```
module rrg_v;
reg [1:0] sel;
reg i0,i1,i2,i3;
wire y;
initial begin
i0=0;
i1=0;
i2=0;
i3=0;
sel=00;
#100;
i0=1;
```

```

i1=0;

i2=0;

i3=0;

sel=01;

#100;

i0=0;

i1=1;

i2=0;

i3=0;

sel=10;

#100;

i0=0;

i1=0;

i2=1;

i3=1;

sel=11;


#100;

end

endmodule

```

Output:-

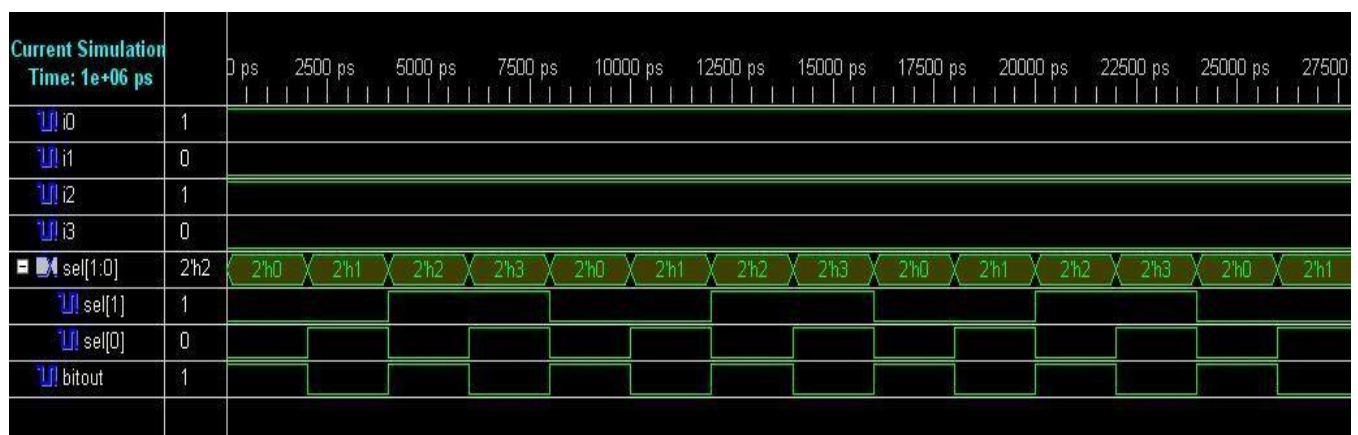

b) 1:4 Demultiplexer :-

Theory :

A 1:4 demultiplexer (DEMUX) is a digital circuit that takes a single input and routes it to one of four output lines based on the values of two selection inputs. It has one data input (D), two selection lines (S_1 , S_0), and four output lines (Y_0 , Y_1 , Y_2 , Y_3). The selection lines determine which output the input will be directed to. For example, if $S_1S_0 = 00$, the input is routed to Y_0 ; if $S_1S_0 = 01$, it goes to Y_1 , and so on. The demultiplexer works by using logic gates, such as AND gates, to direct the input signal to the correct output. It is commonly used in applications where a single data source needs to be distributed to multiple destinations, such as in communication and data processing systems.

 


Figure 3 - 1:4 Demultiplexer

Truth Table :-

Selection Inputs		Outputs			
S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

Demux[1:4]:-

```
module demux(input[1:0] sel,input i,  
Output reg (y0,y1,y2,y3);  
always@(sel,i)  
begin  
case(sel)  
2'b00:{y0,y1,y2,y3}={i,3'b0};  
2'b01:{y0,y1,y2,y3}={1'b0,i,2'b0};  
2'b10:{y0,y1,y2,y3}={2'b0,i,1'b0};  
2'b11:{y0,y1,y2,y3}={3'b0,i};  
default:{y0,y1,y2,y3}={0,0,0,0};  
endcase  
end  
endmodule
```

TestBench:-

```
module ggh_k;  
reg[1:0]sel;  
reg[1:0] i;  
wire y0;  
wire y1;  
wire y2;  
wire y3;  
sdf uut(  
.sel(sel),  
.i(i),  
.y0(y0),  
.y1(y1),  
.y2(y2),  
.y3(y3),);
```


Initial begin

```
Sel=00;
```

```
i=1;
```

```
#100;
```

```
Sel=01;
```

```
i=1;
```

```
#100;
```

```
Sel=10;
```

```
i=1;
```

```
#100;
```

```
Sel=11;
```

```
i=1;
```

```
#100;
```

```
end
```


```
endmodule
```

Output:-



c) BCD to Excess 3 converter and vice versa :

Theory :

 

A **BCD to Excess-3 converter** is a digital circuit that converts a Binary Coded Decimal (BCD) input into an Excess-3 code. In BCD, each decimal digit is represented by a 4-bit binary number, while Excess-3 adds 3 to each decimal digit before encoding it. For example, the BCD representation of the digit "2" is 0010, and in Excess-3, it becomes 0101 (which is 2 + 3). The conversion is achieved by adding the binary value of 3 (0011) to the BCD input.

Conversely, an **Excess-3 to BCD converter** takes an Excess-3 input and subtracts 3 from it to return the original BCD code. For instance, the Excess-3 code for "5" is 1000, and subtracting 3 (0011) gives 0101, which is the BCD for "2". These converters are useful in digital systems that handle decimal numbers, especially in applications like digital clocks, calculators, and other devices that require numeric processing.

Truth Table :

BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

BCD to Excess :-

$$W=A+BC+BD$$

$$X=B'C+B'D+BC'D'$$

$$Y=CD+C'D'$$

$$Z=D'$$

```
module w=(a w BCD_EX3(  
Input b,  
Input c,  
Input d,  
Output w,  
Output x,  
Output y,  
Output z);  
assign w=(a|(b&c)|(b&d);  
assign x=(((~b)&c)&((~b)&d)|(b&(~c)&~d)));  
assign y=((c&d)|((~c)&(~d)));  
assign z=(~d);  
endmodule
```

Test Bench:-

```
module rrg_x;  
reg a;  
reg b;  
reg c;  
reg d;  
wire w;  
wire x;  
wire y;  
wire z;  
rdt uut(  
.a(a),
```

.b(b),

.c(c),

.d(d),

.w(w),

.x(x),

Y(y),

Z(z),

);

Initial begin

a=0;

b=0;

c=0;

d=0;

#100;

a=0;

b=0;

c=0;

d=1;

#100;

a=0;

b=0;

c=1;

d=0;

#100;

a=0;

b=0;

c=1;

d=1;

#100;


a=0;

b=1;

c=0;


```
d=0;
#100;
endmodule
```

Output :-

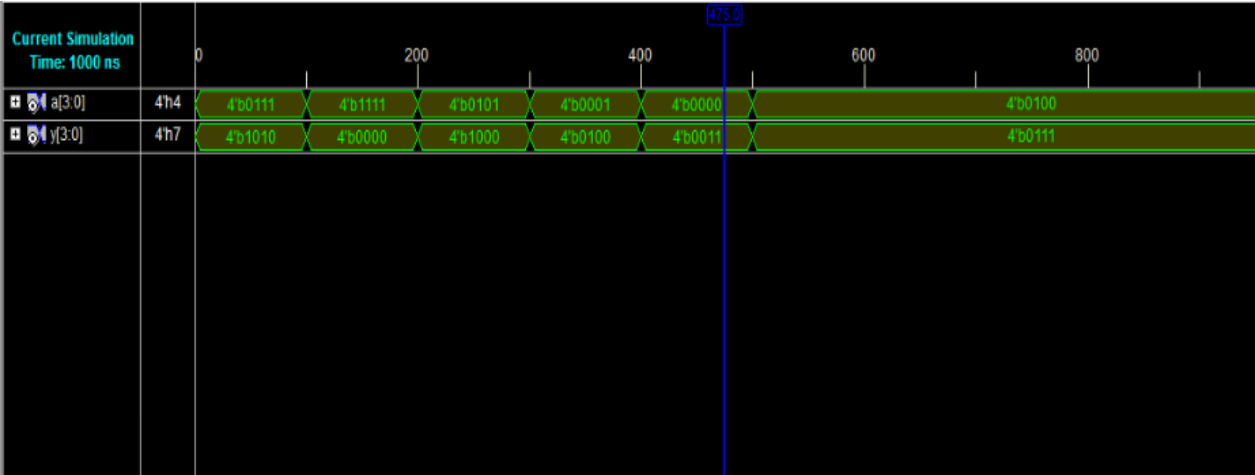

d) Binary to Gray Converter and vice versa :

Theory :

 

Logic Circuit for Binary to Gray Code Converter

Binary to Gray code conversion is a process where a binary number is transformed into its equivalent Gray code. In Gray code, only one bit changes at a time between consecutive numbers, which helps minimize errors in digital communication and electronics. To convert from binary to Gray code, the most significant bit (MSB) remains the same, and each subsequent bit is obtained by XOR-ing the corresponding binary bit with the previous Gray code bit. For example, the binary number 1101 converts to Gray code as 1011.

The **Gray to Binary conversion** is the reverse process, where a Gray code is converted back to its original binary form. To convert from Gray code to binary, the MSB remains unchanged, and each subsequent binary bit is derived by XOR-ing the previous binary bit with the current Gray code bit. This method ensures the accurate recovery of the original binary number. Both conversions are used in applications like error correction, rotary encoders, and digital communication systems.

Truth Table :

Natural-binary code				Gray code			
B3	B2	B1	B0	G3	G2	G1	G0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

BINARY TO GRAY:-

```
module bin2gray(input[3:0] bin,output[3:0]G);  
  
assign G[3]=bin[3];  
assign G[2]=bin[3]^bin[2];  
assign G[1]=bin[2]^bin[1] ;  
assign G[0]=bin[1]^bin[0];  
endmodule
```

Test Bench:-

```
Module sst_s; reg [3:0] bin;  
wire[3:0]G; sdf uut(  
.bin(bin),  
.G(G),  
);  
Initial begin  
  
bin=0100;  
  
#100;  
bin=1001;  
  
#100;  
Endmodule
```

Output :-



M	Q ₃	Q ₂	Q ₁	Q ₃ [*]	Q ₂ [*]	Q ₁ [*]	T ₃	T ₂	T ₁
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	0	1	0	0	0	1

SYNCHRONOUS UPORDOWN COUNTER:-

```
module upordown_counter(clk,rst,upordown,count);

input clk,rst,upordown;
output [3:0] count;
reg [3:0] count=0;
always@(posedge (clk) or posedge(rst))
begin
if(reset==1)
count<=0;
else
if(upordown==1)
if (count==15)
count<=0;
else
count<=count+1;
else
if (count==0)
count<=15;
else
count<=count-1;
end
endmodule
```

TestBench:-

```
Module tdc_r;
reg clk;
reg rst;
reg upordown;
wire [3:0] count;
pqr uut(
```

```

.clk(clk),
.rst(rst);
.upordown(upordown),
.count(count),
);
always#10 clk=~clk;
Initial begin
clk=0; rst=0;
upordown=0;
#100;
clk=0;
upordown=1;
#100;
Clk=0;
upordown=0;
#100;
endmodule

```

Output:-




EXPERIMENT NO :- 07

a) 4-Bit Universal Shift

Register :-

Theory :-

A **4-bit Universal Shift Register** is a versatile digital storage device capable of shifting data in both directions (left and right), loading data in parallel, and holding data. It consists of four flip-flops, and each flip-flop can store one bit of data. The register allows for different operations based on control inputs: data can be shifted left or right with each clock pulse, new data can be loaded in parallel, or the current data can be retained without change. The shift operations are controlled by shift direction and shift enable signals, while the parallel load operation is controlled by a load signal. This flexibility makes the universal shift register ideal for applications requiring data storage, transfer, and manipulation, such as in data conversion, temporary storage in digital circuits, and serial-to-parallel or parallel-to-serial conversion.

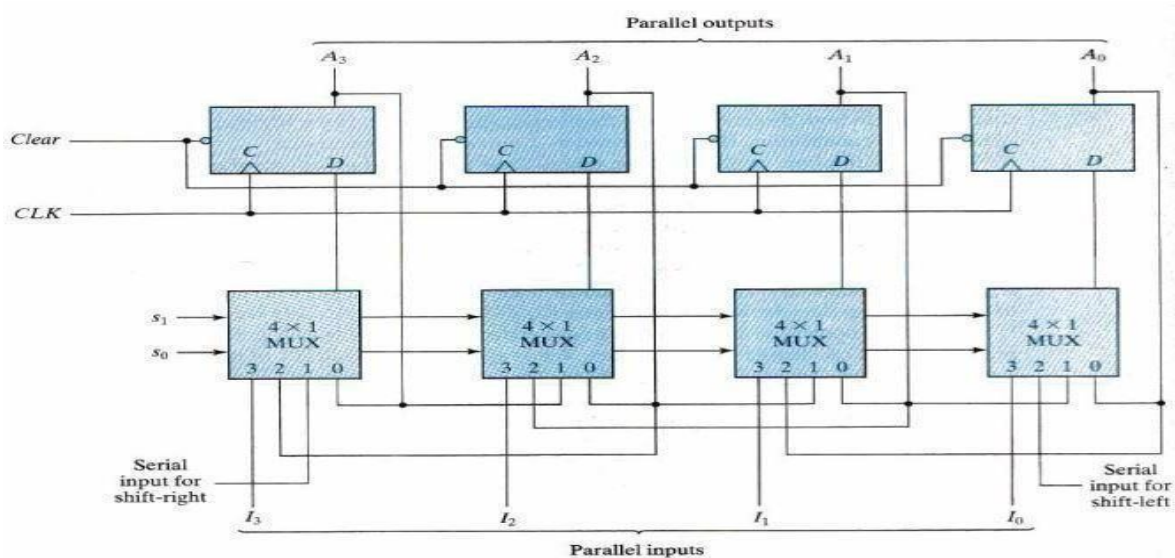

Truth Table :-

S1	s0	Register operation
0	0	No changes
0	1	Shift right
1	0	Shift left
1	1	Parallel load

UNIVERSAL SHIFT REGISTER:-

```
module universal_shift_reg(  
    input clk,rst_n,  
    input[1:0] select,  
    input[3:0] p_in;  
    input s_left_in,  
    input s_right_in,  
    output reg[3:0] p_out,  
    output s_left_out,  
    output s_right_out);  
    always@(posedge clk)  
    begin  
        if(!rst_n)  
            p_out<=0;  
        else begin  
            case(select)  
                2'b01:p_out<={s_right_in,p_out[3:1]};  
                2'b10:p_out<={p_out[2:0],s_left_in};  
                2'b11:p_out<=p_in; default:p_out<=p_out;  
            endcase  
        end  
        end  
        assign s_left_out=p_out[0];  
        assign s_right_out=p_out[3];  
    endmodule
```

Test Bench:-

```
module ccf_i;
    reg clk;
    reg rst_n;
    reg [1:0]select;
    reg[3:0]p_in; reg
    s_left_in; reg
    s_right_in; wire
    [3:0] p_out; wire
    s_left_out;
    wire s_right_out);
    always#10 clk=~clk
    initial begin
        clk=0;
        rst_n=0;
        select=0;
        p_in=0;
        s_left_in=0;
        s_right_in=0;
        #100;
        clk=0; rst_n=1;
        select=2'b11;
        p_in=4'b1101;
        s_left_in=1'b1;
        s_right_in=1'b0;
        #100;
        clk=0;
        rst_n=1;
        select=2'b10;
```

```

p_in=4'b1101;
s_left_in=1'b1;
s_right_in=1'b0;
#100;
endmodule

```

Output:-





EXPERIMENT NO :- 08

Seven-Segment Light-Emitting Diode (LED) Display



Theory :-

The seven-segment displays are designed for displaying numeric values. You can find them anywhere from instruments to space shuttles. They are the most practical way to display numeric values. They are cheap and easy to use. Not only that, they are highly readable in any light condition, unlike LCDs. You can find them in many everyday usages like counters or token systems, etc. And here is a small simulation showing the Seven Segment Interface. The Arduino will count from 0 to 9 and repeat. The value will be displayed on the Seven Segment display. Seven-segment displays are available in various sizes and colours. They are available from 0.28 inches to 18 inches, and even bigger sizes are available for industrial usage. The **most commonly used display size is 0.56 inches**.

  

Now let's see how we can drive a seven-segment display with an Arduino. For that let's start by placing the display module on a breadboard with the decimal point facing downwards. Then wire up each pin as per the connection diagram below. In this tutorial, we will be using a Common Cathode display. Connect either of the common pins (seven-segment pin 3 or 8) to the ground. And connect the rest of the pins to D2 to D9 of the Arduino through a current limiting resistor, as per the connection diagram. Just like driving an LED, it is preferable to use these current limiting resistors to increase the display life. Choose these values depending on the display colour and size. Here we will be using a 330 ohms resistor which will provide around 10mA current for the LEDs.

And here is the actual circuit.

  


```

#include "SevSeg.h"

SevSeg sevseg;

void setup()
{
    //Set to 1 for single-digit display

    byte numDigits = 1;

    //defines common pins while using multi-digit display. Left for single digit display

    byte digitPins[] = {};

    //Defines Arduino pin connections in order: A, B, C, D, E, F, G, DP

    byte segmentPins[] = {9,8, 7, 6, 5, 4, 3, 2};

    byte displayType = COMMON_CATHODE; //Use COMMON_ANODE for Common Anode display

    bool resistorsOnSegments = true; //'false' if resistors are connected to common pin

    //Initialize sevseg object. Use COMMON_ANODE instead of COMMON_CATHODE for CA display

    sevseg.begin(displayType, numDigits, digitPins, segmentPins, resistorsOnSegments);

    sevseg.setBrightness(90);
}

void loop()
{
    //Display numbers 0-9 with 1 seconds delay

    for(int i = 0; i <= 10; i++)

    {
        if (i == 10)

        {
            i = 0;
        }

        sevseg.setNumber(i);

        sevseg.refreshDisplay();

        delay(1000);

    }
}

```

EXPERIMENT NO:9

Data Flow and Structural Modeling

Data flow modeling of Half Adder:

```
module half_adder(a, b, sum, carry);  
  
input a, b;  
  
output sum, carry;  
  
assign sum = a ^ b;  
  
assign carry = a & b;  
  
endmodule
```

Structural modeling of Half Adder:

```
module half_adder(a, b, sum, carry);  
  
input a, b;  
  
output sum, carry;  
  
xor (sum, a, b);  
  
and (carry, a, b);  
  
endmodule
```

Data flow modeling of Full Adder:

```
module full_adder(a, b, cin, sum, carry);  
  
input a, b, cin;  
  
output sum, carry;  
  
assign sum = a ^ b ^ cin;  
  
assign carry = (a & b) | (b & cin) | (cin & a);  
  
endmodule
```

Structural modeling of Full Adder:

```
module fulladder(a, b, cin, sum, carry);  
  
input a, b, cin;  
  
output sum, carry;  
  
wire w1, w2, w3, s1;  
  
xor x1(s1, a, b);  
  
xor x2(sum, s1, cin);  
  
and a1(w1, a, b);  
  
and a2(w2, b, cin);  
  
and a3(w3, a, cin);  
  
or o1(carry, w1, w2, w3);  
  
endmodule
```